



End Term (Odd) Semester Examination November 2025

Roll no.....

Name of the Course and semester: B.Tech IIIrd sem

Name of the Paper: Digital System Design

Paper Code: TEC 302

Time: 3 hour

Maximum Marks: 100

Note:

- (i) All the questions are compulsory.
- (ii) Answer any two sub questions from a, b and c in each main question.
- (iii) Total marks for each question is 20 (twenty).
- (iv) Each sub-question carries 10 marks.

Q1. (2X10=20 Marks)

- a. Explain the concept of signed binary numbers. Perform the following operations and show all steps:
 $(-35)_{10} + (27)_{10}$, using 8-bit 2's complement arithmetic. (CO1)
- b. Convert the following in required base (CO1)
 $(56)_8 = (\quad)_5 = (\quad)_{16}$
- c. Write short notes on: (i) Binary Codes (ii) Error detection using parity bit. (CO1)

Q2. (2X10=20 Marks)

- a. Minimize the Boolean function $F(A,B,C,D,E) = \Sigma(0,2,4,8,9,10,12,13,15,19,21,23,25,27,29,31)$ using a 5-variable K-map. (CO2)
- b. Explain Boolean theorems and postulates. Prove DeMorgan's theorems. (CO2)
- c. Simplify the Boolean function $F(A,B,C,D) = \Sigma(0,1,2,5,8,9,10,13)$ using Quine Mccluskey method. (CO2)

Q3. (2X10=20 Marks)

- a. Draw and explain circuit of Decimal adder. (CO3)
- b. Design a 4:16 decoder using 2:4 decoders. (CO3)
- c. Implement Full adder using Demultiplexer. (CO3)

Q4. (2X10=20 Marks)

- a. Explain operation of SISO shift register. (CO4)
- b. Design a MOD-5 Asynchronous counter. (CO4)
- c. Convert JK Flip Flop into D Flip Flop. (CO4)

Q5. (2X10=20 Marks)

- a. Explain Verilog modeling styles and data types with examples. (CO5)
- b. Write Verilog code for 4×1 multiplexer using case statement. (CO5)
- c. Write Verilog code to model a 4-bit adder. (CO5)