



Term Evaluation (Odd) Semester Examination September 2025

Name of the Course: Bachelor of Computer Applications
Semester: IIIrd
Name of the Paper: Digital Logic Design
Paper Code : TBC 303

Roll no.

Time: 1.5 hour

Maximum Marks: 50

Note:

- (i) Answer all the questions by choosing any one of the sub-questions
- (ii) Each question carries 10 marks.

Q1.

(10 Marks)
(CO1)

a. Perform following conversions

- (i) $(110101)_2 \rightarrow (\quad)_{10}$
- (ii) $(737)_8 \rightarrow (\quad)_2$
- (iii) $(CF3)_{16} \rightarrow (\quad)_8$
- (iv) $(245)_{10} \rightarrow (\quad)_{16}$

OR

b. Perform the subtraction $(110011)_2 - (101001)_2$ using 2's complement method and verify the result using direct binary subtraction. (CO1)

Q2.

(10 Marks)
(CO2)

a. Simplify the Boolean expression using theorems only

$$Y = AB + ABCD' + ABC' + ABC'D'$$

OR

b. Express the following function in canonical SOP and POS form (CO1)

$$Y = A + B'C$$

$$Y = (A+B)(A+C')$$

Q3.

(10 Marks)

a. Represent the decimal number 130 in BCD and Gray code. Verify that the Gray code is known as unit distance code. (CO1)

OR

b. Minimize the following Boolean function using K-map method: (CO2)

$$F(A,B,C,D) = \sum m(0,2,3,8,10,11,12,14)$$

Q4.

(10 Marks)

a. Prove NAND is a universal gate by implementing all basic gates using only NAND gate. (CO2)

OR

b. Use K-map to minimize: (CO2)

$$F(A,B,C,D) = \pi M(1,2,3,7,8,9,11,15)$$

Q5.

(10 Marks)
(CO2)

a. Realize the following Boolean expression using only NAND gates:

$$F(A,B,C) = AB' + A'C$$

OR

b. Prove Demorgan's theorem with the help of truth tables. (CO2)