

End Term (Odd) Semester Examination December 2025

Roll no.....

Name of the Course and semester: Electronics & Communication/ 3rd semester

Name of the Paper: Network Theory

Paper Code: TEC -303

Time: 3 hour

Maximum Marks: 100


Note:

- (i) All the questions are compulsory.
- (ii) Answer any two sub questions from a, b and c in each main question.
- (iii) Total marks for each question is 20 (twenty).
- (iv) Each sub-question carries 10 marks.

Q1.

(2X10=20 Marks)

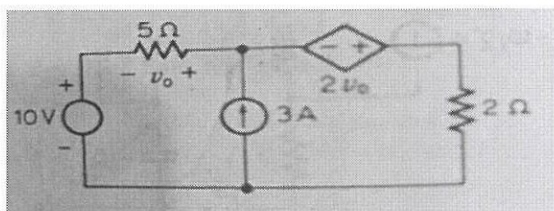- a. State and explain Millmans theorem with suitable example (CO: 1)
- b. For the circuit given below find the current in 2 ohm resistor using Nortons theorem. (CO: 2)




- c. Illustrate Tellegens theorem and explain it with suitable exam. (CO:1)

Q2.

(2X10=20 Marks)

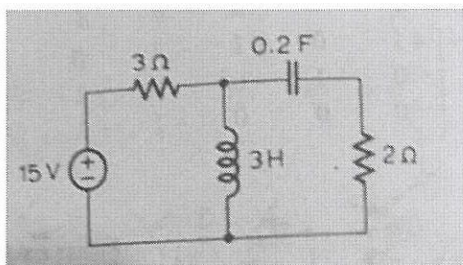- a. Explain the concept of Duality in graph theory also draw the Dual for the Network given below: (CO: 2)






End Term (Odd) Semester Examination December 2025


b. For obtain the Tie set matrix for the circuit given below:

(CO: 2)

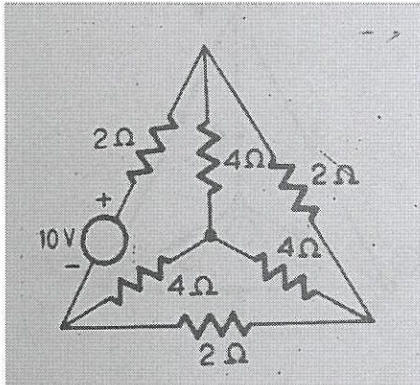

c. Draw the graph of the network shown below. How many trees are possible for this graph? Draw any two of your choice.

(CO: 2)

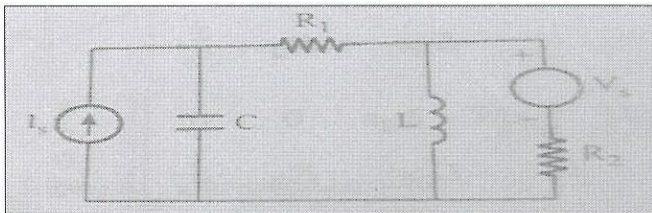

Q3.

(2X10=20 Marks)

a. Derive the condition of reciprocity and Symmetry for Y parameters.

(CO: 4)

b. Perform the following conversions:


(CO: 4)

i) Z to Y parameters

ii) Y to H parameters

c. Find Z parameter for the network shown below:

(CO: 4)

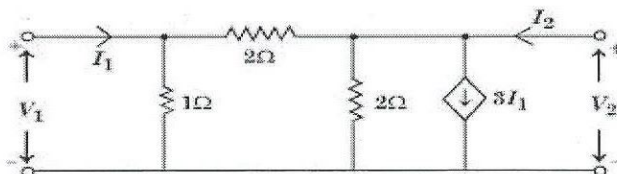



End Term (Odd) Semester Examination December 2025

Q4. (2X10=20 Marks)

- a. Realize the following RC driving point impedance function in First Foster form:

$$Z(s) = (s^2 + 6s + 8) / (s^2 + 4s + 3) \quad (\text{CO: 5})$$

- b. Obtain Cauer-I form for the function given by: (CO: 5)


$$Z(S) = (6s^3 + 15s) / (s^2 + 2)$$

- c. Obtain Cauer -II form for :

$$Z(S) = (s^4 + 7s^2 + 8) / (3s^3 + 12s) \quad (\text{CO: 5})$$

Q5. (2X10=20 Marks)

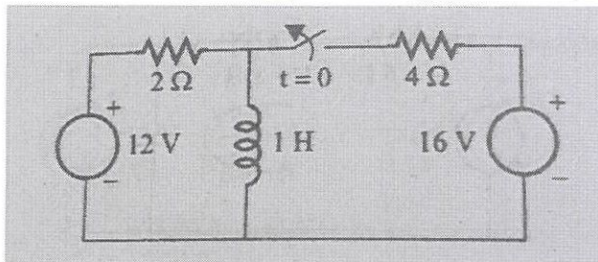- a. Define poles and zeros of a transfer function. How do the locations of poles and zeros on the s-plane affect the system's stability and frequency response? (CO: 3)
- b. Find $i(t)$ for $t > 0$ in the circuit shown below. Switch is opened at $t = 0$ (CO: 4)



C. Discuss the properties of the following: (CO: 2)

- i) Driving Point Function
- ii) Transfer function