



## End Term (Odd) Semester Examination November 2025

Roll no.....

Name of the Course and semester: B.Tech ECE (III)

Name of the Paper: Electronic Devices and Circuits

Paper Code: TEC 301

Time: 3 hour

Maximum Marks: 100

### Note:

- (i) All the questions are compulsory.
- (ii) Answer any two sub questions from a, b and c in each main question.
- (iii) Total marks for each question is 20 (twenty).
- (iv) Each sub-question carries 10 marks.

Q1.

(2X10=20 Marks) CO1

- a. Explain the formation of n type and p type semiconductors. Establish a relation between charge densities in both n type and p type semiconductors.
- b. Derive an equation for drift current in conductors. What is diffusion current. Write down its equation for n type and p type semiconductors.
- c. What is the Hall effect? Derive the expression for the Hall coefficient and discuss its applications in semiconductor device characterization.

Q2.

(2X10=20 Marks) CO2

- a. Explain the formation of depletion region in PN junction diode. Explain the working of pn junction diode with the help of V-I diagram.
- b. Explain the working of clipper and clamper circuit with the help of a diagram.
- c. What is Zener breakdown. Explain the use of Zener diode as voltage regulator in a circuit with fixed load and supply voltage.

Q3.

(2X10=20 Marks) CO3

- a. Explain the working of Common Emitter configuration of BJT with its input and output characteristics.
- b. Draw the small signal model of CE configuration of BJT and derive the equation for voltage gain.
- c. What is early effect in BJT. Explain the working of BJT as a switch.

Q4.

(2X10=20 Marks) CO4

- a. What is field effect transistors. Explain the working of JFET in detail with suitable diagram.
- b. Draw the small signal model of CS configuration of JFET and derive formula for gain.
- c. Draw the small signal model of CD configuration of JFET and derive formula for gain.

Q5.

(2X10=20 Marks) CO5

- a. Explain the working of enhancement type MOSFET in detail with the help of suitable diagram.
- b. Explain the working of depletion type MOSFET in detail with the help of suitable diagram.
- c. Derive the relation between V-I characteristics of depletion type MOSFET.

Note For the question paper setters:

- Question paper should cover all the COs of the course.
- Please specify COs against each question.