



Term Evaluation (Odd) Semester Examination September 2025

Roll no.

Name of the Course: B.Tech

Semester: I

Name of the Paper: Basic Electrical Engineering

Paper Code: TEE 101

Time: 1.5 hour

Maximum Marks: 50

Note:

- (i) Answer all the questions by choosing any one of the sub-questions
- (ii) Each question carries 10 marks.

Q1.

(10 Marks) (CO1)

a. Define the following terms along with suitable examples:

- (i) Unilateral and Bilateral Elements
- (ii) Active and Passive Elements
- (iii) Linear and Non-linear elements
- (iv) KCL & KVL

OR

b. Find the total resistance between the terminals "a" and "b" of the circuit shown in fig. 1

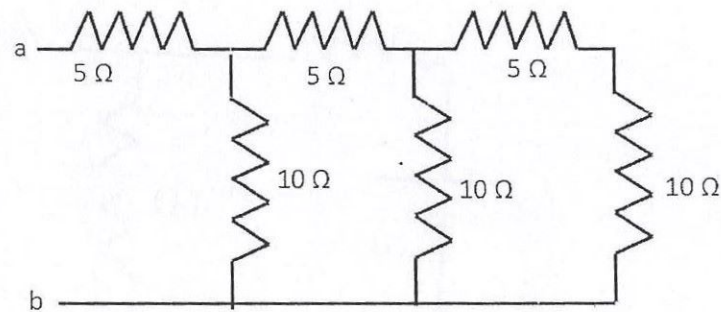


Fig. 1

Q2.

(10 Marks) (CO1)

a. Find out Nodal voltages and current flowing from V_1 to V_2 in the circuit shown in fig 2 (a) with the help of Nodal analysis.

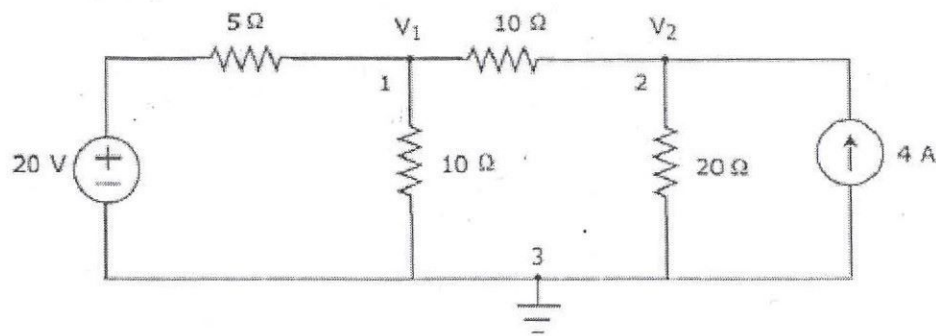


Fig. 2(a)

Term Evaluation (Odd) Semester Examination September 2025

OR

- b. Find out mesh currents and current in R_2 resistance for the given electrical circuit shown in fig. 2 (b) using mesh analysis.

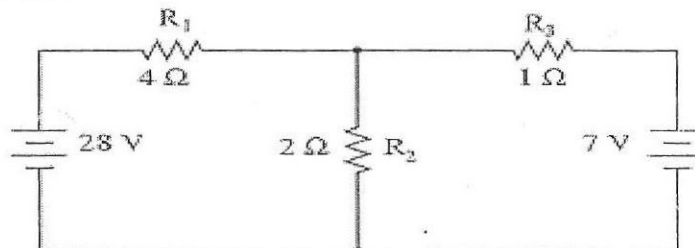


Fig. 2(b)

Q3.

(10 Marks) (CO1)

- a. Define Thevenin's Theorem. Describe the steps to solve an electric network using Thevenin theorem.

OR

- b. Calculate the current through 4Ω resistance in the given network shown in fig. 3 using Thevenin's Theorem.

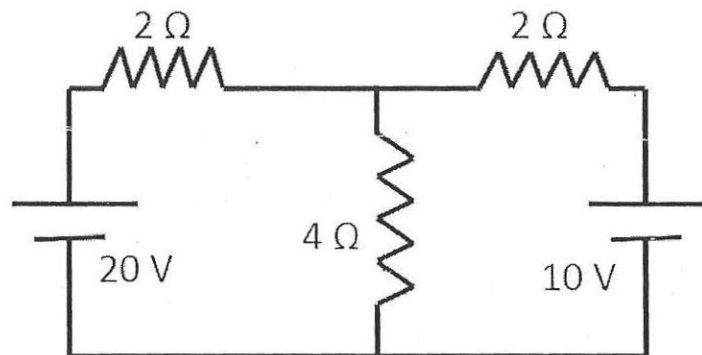


Fig 3

Q4.

(10 Marks) (CO1)

- a. Determine the current in the branches of the network shown in fig 4(a) using Superposition Theorem.

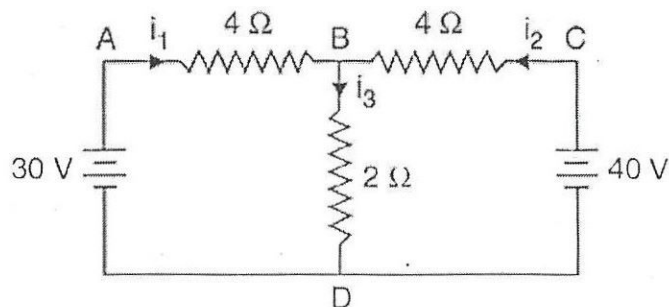


Fig. 4(a)

Term Evaluation (Odd) Semester Examination September 2025

OR

- b. Find out current in 5Ω resistor with the help of Norton's Theorem in the circuit shown in fig 4(b).

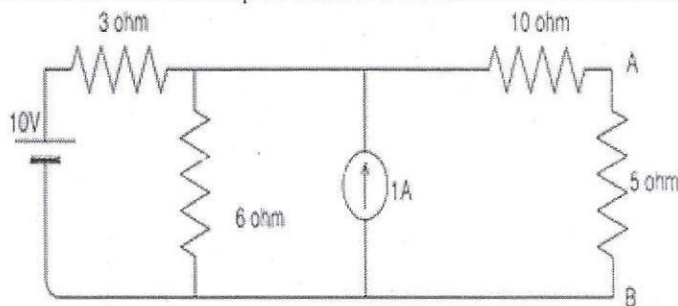


Fig 4(b)

Q5.

(10 Marks) (CO1)

- a. Fig. 5(a) shows one node of an electric circuit. Find v_2 .
Given $i_1 = 4A$, $v_3 = 3V$, $v_4 = 8V$

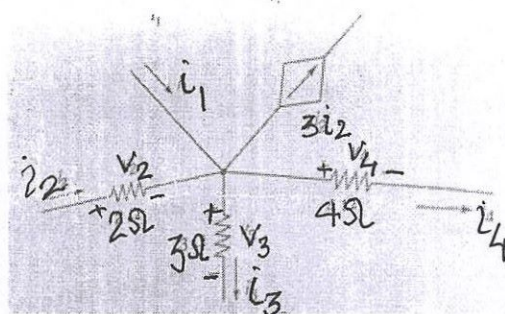


Fig. 5(a)

OR

- b. Consider the loop in fig. 5 (b) which forms part of an electric circuit. Find i_4 .
Given $v_1 = 6V$, $i_2 = 2A$, $i_3 = 4A$

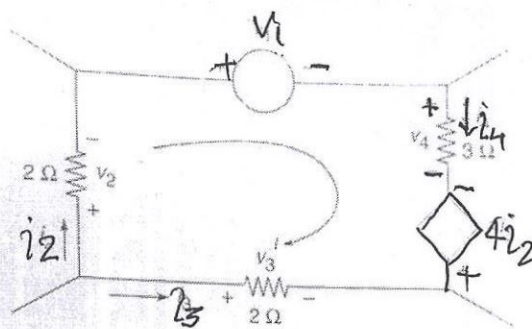


Fig. 5(b)