



Term Evaluation (Even) Semester Examination March 2025

Roll no.

Name of the Course: B.Tech.(ME)

Semester: IV

Name of the Paper: Mechatronics

Paper Code: TME 409

Time: 1.5 hour

Maximum Marks: 50

Note:

- (i) Answer all the questions by choosing any one of the sub-questions
- (ii) Each question carries 10 marks.

Q1.

CO 1 (10 Marks)


- a. Enlist various components of a mechatronic system? Discuss with the help of block diagram.
- OR
- b. Draw the circuit of an op-amp inverting amplifier, and derive the expression for its voltage gain.

Q2.

CO 1 (10 Marks)

- a. What do you mean by CMRR, slew rate and input offset voltage of an op-amp? Write the characteristics of an ideal op-amp.
- OR

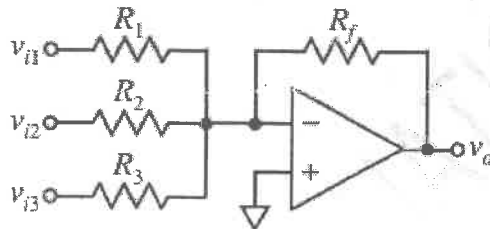- b. Obtain the expression of output of following circuit:



Q3.

CO 2 (10 Marks)

- a. Draw the block diagram of a data acquisition system. Discuss the role and working of multiplexers in it.
- OR
- b. Draw the circuit of an instrumentation amplifier. Derive the expression for its output.

Q4.

CO 2 (10 Marks)

- a. Draw the circuit of an R-C low pass filter. Derive the expression for its frequency response, and plot it.
- OR
- b. (i) An RC high pass filter is formed with $R = 5 \text{ k}\Omega$, and $C = 15 \text{ }\mu\text{F}$. Determine its cut-off frequency in Hertz.
(ii). Discuss how a bandpass filter can be designed?

Q5.

CO 2 (10 Marks)

- a. Describe the role of A/D converter in a mechatronic system? Discuss how A/D conversion is performed?
- OR
- b. Consider a 4 bit D/A converter with reference voltage of 5 V. Draw its circuit and determine its resolution. Also find its output voltage for input 1001.